Electricity: Cells

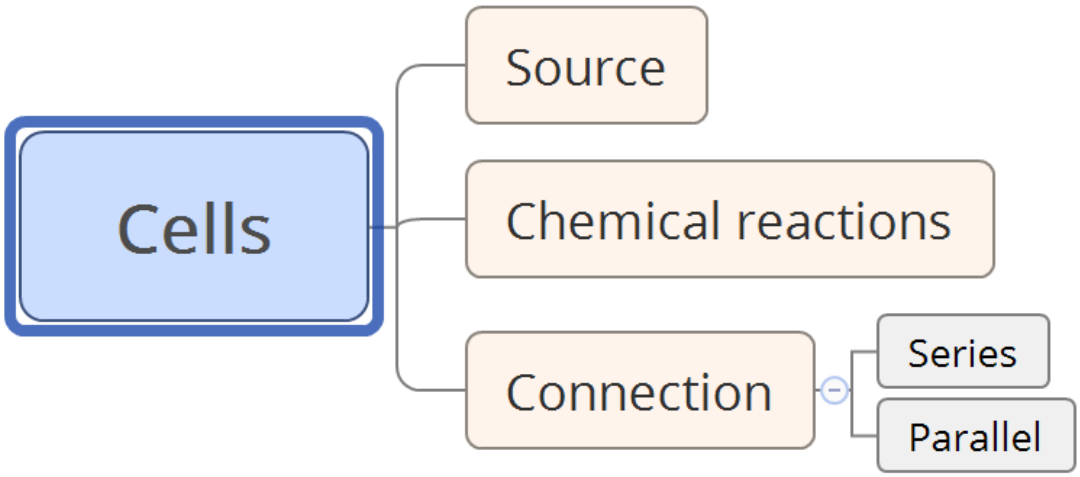

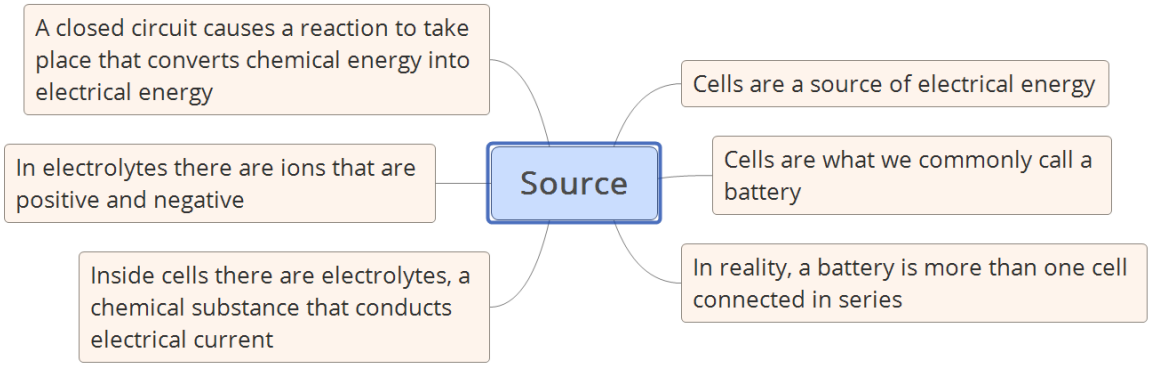

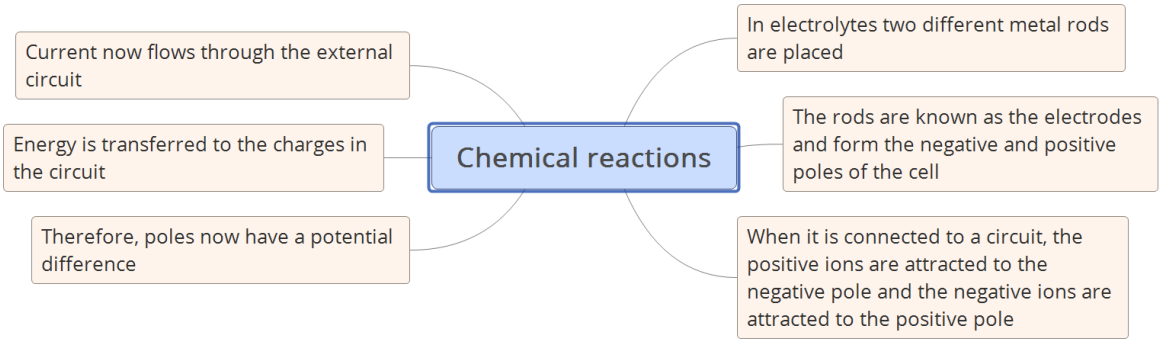

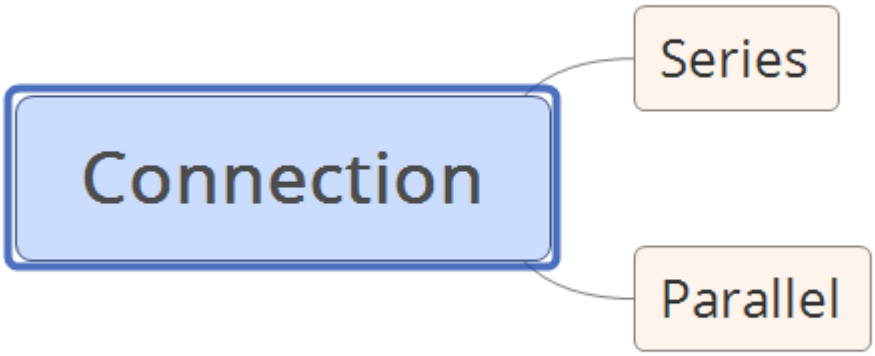
Connection
Series
Parallel

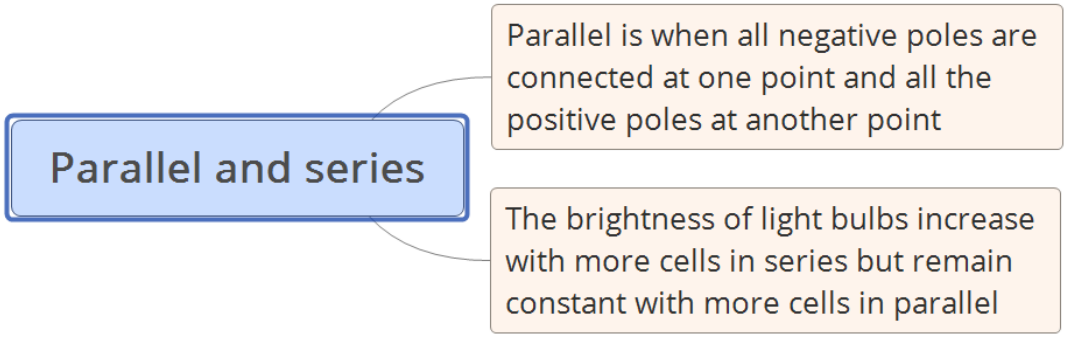
Parallel and series
Parallel is when all negative poles are connected at one point and all the positive poles at another point
The brightness of light bulbs increase with more cells in series but remain constant with more cells in parallel